

ISTANBUL TECHNICAL UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BLG 222E
Computer Organization
Project 1

PROJECT DATE : 12.04.2023

GROUP MEMBERS:

number : name

150220762 : Muhammed Yusuf Mermer

150210071 : Emre Çamlıca

SPRING 2023

Contents

1 INTRODUCTION

2 IMPLEMENTATIONS AND EXPLANATIONS

2.1 Part 2

2.1.1 Part 2.c

In part 2c, we implemented Address Register File (ARF) using registers we implemented at very beginning. As a parameter values, we gave registers 8 bits as 8 bit is necessary for implementing PC, AR, SP and PCPrev. Besides, of enable and clock these registers already supports funsel and load capabilities, which works as specified in part 2.a. Therefore, we can directly send clock, funsel and load informations coming from input of this module to these registers without writing them again explicitly.

However, for the rsel, like in the part 2.b we will send individual bits to the enables of the registers. As in the instruction, if a bit coming to the enable is 1, then operation declared by funsel will be done.

All 8-bit of information coming from these registers are connected to 16 multiplexers.

First 8 of them used for getting result of outA and other 8 used for getting result of outB. Which of these groups takes inputs with same patterns.

What these multiplexers do is that they take significantly same digits of different registers as inputs and output the bit of a register that wanted by outasel or outbsel. As specified in the part 2.c; 00 gives AR's bits, 01 SP's bits, 10 PCPrev's bits, 11 PC's bits. These two 8 bits coming from multiplexers concatenated in outa and outb and gave as the output of the module.

inputs: clk(1 bit), load(8 bits), outasel(2 bits), outbsel(2 bits), funsel(2 bits), rsel(4 bits)

outputs: outa(8 bits), outb(8 bits)

module name: arf

2.2 Part 3

I designed the required functions of the ALU for each FunSel case. The functions corresponding to each case will be discussed in the sub-sections. I defined 4 extra variables that made it easier to design the arithmetic functions. These variables are basically the 9 bit representations of A , B , \overline{B} and the result "out" of the corresponding arithmetic operation, with the 9'th bits of A , B and \overline{B} set to 0 to correctly represent arithmetic operations using 8 bits in verilog.

I used an always block to be able to change outputs whenever a different input is given

and inside of it, I used "case" statement to give the outputs corresponding to each FunSel input. The registers are never reset and their states change only when they are allowed to.

Before explaining each funsel case, I will talk about the certain patterns I use to check N, Z and C flags whenever it is necessary. For the N flag, I assign the most significant bit of the OutALU to Flag[1], which indicates the sign bit of a binary number. For the Z flag, I check whether the OutALU is composed of full of 0's. For the C flag in arithmetic operations I check the most significant bit of the out variable, which is a 9 bit register to store the result of arithmetic operations; in shift operations I check the disappearing bits of A after doing the shift operation. That is, the most significant bit for the right shift and the least significant one for the left shift. Checking the overflow flag is basically done by checking the changes in the most significant bit. I will discuss each of them in the following sub-sections, as it is done differently for each operation.

2.2.1 FunSel=0000

OutALU is assigned to A , then the necessary flags are set.

2.2.2 FunSel=0001

OutALU is assigned to B , then the necessary flags are set.

2.2.3 FunSel=0010

OutALU is assigned to \overline{A} , then the necessary flags are set.

2.2.4 FunSel=0011

OutALU is assigned to \overline{B} , then the necessary flags are set.

2.2.5 FunSel=0100

The result of the addition of 9 bit versions of A and B is assigned to the 9 bit variable *out*. The carry flag is checked afterwards, if it is 1, the *out* is incremented by one. After that the necessary flags are set.

When adding two binary numbers an overflow can occur only when the two numbers have the same sign, denoted by $A[7] \wedge B[7]$. We can understand that an overflow occurred when the result is different than the signs of the operands. We can logically express this condition as $(A[7] \wedge B[7]) \oplus OutALU[7]$, a logic one result indicating that an overflow occurred.

2.2.6 FunSel=0101

The result of the addition of 9 bit versions of A and \overline{B} is assigned to the 9 bit variable *out* with the addition of binary 1. After that the necessary flags are set.

When subtracting two binary numbers an overflow can occur only when the two numbers have different signs, denoted by $A[7]^B[7]$. We can understand that an overflow occurred when the result is different than the sign of the first operand, A , since subtracting a number with a different sign should always result in a number having the same sign as the first operand. We can denote this condition by $A[7] \oplus OutALU[7]$. We can combine the two logic expressions we formed by "and"ing them to create a logic expression for overflow, which can be written as $(A[7] \oplus B[7]) \wedge (A[7] \oplus OutALU[7])$, a logic one result indicating that an overflow occurred.

2.2.7 FunSel=0110

For the "compare" function, the "subtraction" operation explained in the previous sub-section is used with the corresponding flags. However this time the result of the subtraction is interpreted considering the flags to give the required output. The function interprets the result using if/else statements. In the if statements the possible cases indicating $A > B$ are checked and the OutALU is set as A if the condition is true, else OutALU is set as full of 0's.

The first possibility indicating $A > B$ is that there is no overflow, the result is not negative and it is not zero, implying that $A - B > 0$. This is denoted by the logic expression $\overline{Flag[0]} \wedge \overline{Flag[1]} \wedge \overline{Flag[3]}$.

The second possibility indicating $A > B$ is that there is overflow and A is positive. Which implies that B is negative. This is denoted by the logic expression $Flag[0] \wedge \overline{A[7]}$.

All other combinations of flag outputs imply that either $B > A$ or $A = B$, which will result in a 0 output.

2.2.8 FunSel=0111

The result of the "bitwise and" operation on A and B is assigned to OutALU, then the necessary flags are set.

2.2.9 FunSel=1000

The result of the "bitwise or" operation on A and B is assigned to OutALU, then the necessary flags are set.

2.2.10 FunSel=1001

The result of the "bitwise nand" operation on A and B, done by negating every bit of $A \wedge B$ is assigned to OutALU, then the necessary flags are set.

2.2.11 FunSel=1010

The result of the "bitwise xor" operation on A and B is assigned to OutALU, then the necessary flags are set.

2.2.12 FunSel=1011

The result of "logic shift left" operation by 1 bit on A is stored in OutALU. After that the necessary flags are set.

2.2.13 FunSel=1100

The result of "logic shift right" operation by 1 bit on A is stored in OutALU. After that the necessary flags are set.

2.2.14 FunSel=1101

The result of "logic shift left" operation by 1 bit on A is stored in OutALU. After that the necessary flags are set.

Here, if The most significant bit of OutALU is not the same as that of A's an overflow flag is raised. This is denoted by the logic expression $A[7] \oplus OutALU[7]$, a logic 1 result indicating that an overflow occurred.

2.2.15 FunSel=1110

The result of "logic shift right" operation by 1 bit on A is stored in OutALU. Then, the most significant bit of OutALU is set equal to the most significant bit of A as expected to prevent overflow. After that the zero flag is set.

2.2.16 FunSel=1111

The result of "logic shift right" operation by 1 bit on A is stored in OutALU. The least significant bit of A is assigned to the most significant bit of OutALU so that the circular shift is done correctly. After that the necessary flags are set.

2.2.17

inputs: A(8 bits), B(8 bits), Funsel(4 bits)

outputs: Flag(4 bits), OutALU(8 bits)

module name: alu

2.3 Part 4

In this part, our purpose is to combine all previously made modules. At first we started with adding memory module that provided. We see that when we are in the write mode it gives high impedance as output and in the read mode we cannot change what is inside of memory.

Our first thought about this is we will write a test bench, so that IR will not take input from memory when memory is in the write mode. Not only IR but also two Multiplexer is also taking input from memory which we want to avoid when memory is in writing mode. We did not implement our test bench because we saw that test bench is already shared one day later (the day we were thinking to start implementing).

After adding module of memory, we defined wires that comes into/ goes out of memory. Address and outALU is not currently output of any other module.

At first we did not thought that nearly every wires have to be sensed as output as test bench required. Therefore, initially we made them as intermediate wires. Then after we see the output wire names, we changed nearly all our wires' name and make them output.

For the connection of IR, we gave 8 least significant bits to the Multiplexer A. At our initial design we output IR's most significant 8 bits from system but later we change it so that it outputs all 16 bits as outputs.

After IR, we add modules of Multiplexer A and Multiplexer B. Even though Multiplexer is already implemented for previous parts, we cannot use them directly because they are just 1 bit which in case of use, make our module complicated. Hence, we made another module for four to one Multiplexer which takes and gives 8 bit values. Not only four two one multiplexer, but also two to one multiplexer which also processing 8 bit values had been made to use on multiplexer C.

After connecting relevant wires to multiplexers, we added ARF to the system. We add new inputs to the system so that we can modify outputs of the ARF.

With the addition of this module we see that order of call of modules inside of another module does not important if there is exist intermediate signals (wires), because ARF depends on memory via multiplexer and memory depends on ARF through memory address information.

Later we add register file and multiplexer C to the system. And we made the connections.

For the ALU at first we make sepearated flag register but due to input and outputs of ALU is strictly given, we cannot write sepearated cin input for ALU which directed us to use a register inside of ALU module for flag. Then we made proper input and output connections to the ALU module.

inputs: ARFOutASel(2 bit), ARFOutBSel(2 bit), IRFunsel(2 bit), ARFFunSel(2 bit), RFFunSel(2 bit), ALUFunSel(4 bit), RFRSel(4 bit), ARFRSel(4 bit), Clock(1 bit), MemWR(1 bit), MemCS(1 bit), IREnable(1 bit), IRLH(1 bit), MuxASel(2 bit), MuxBSel(2 bit), MuxCSel(1 bit), RFOutASel(3 bit), RFOutBSel(3 bit), RFTSel(4 bit)

outputs: AOut (8 bits), BOut (8 bits), ALUOut (8 bits), ALUOutFlag (4 bits), ARFAOut (8 bits), Address (8 bits), MemoryOut (8 bits), MuxAOut (8 bits), MuxBOut (8 bits), MuxCOut (8 bits), IROut (16 bits)

module name: ALUSystem

3 DESIGN PHOTOS

3.1 Part 2

3.1.1 Part 2.c

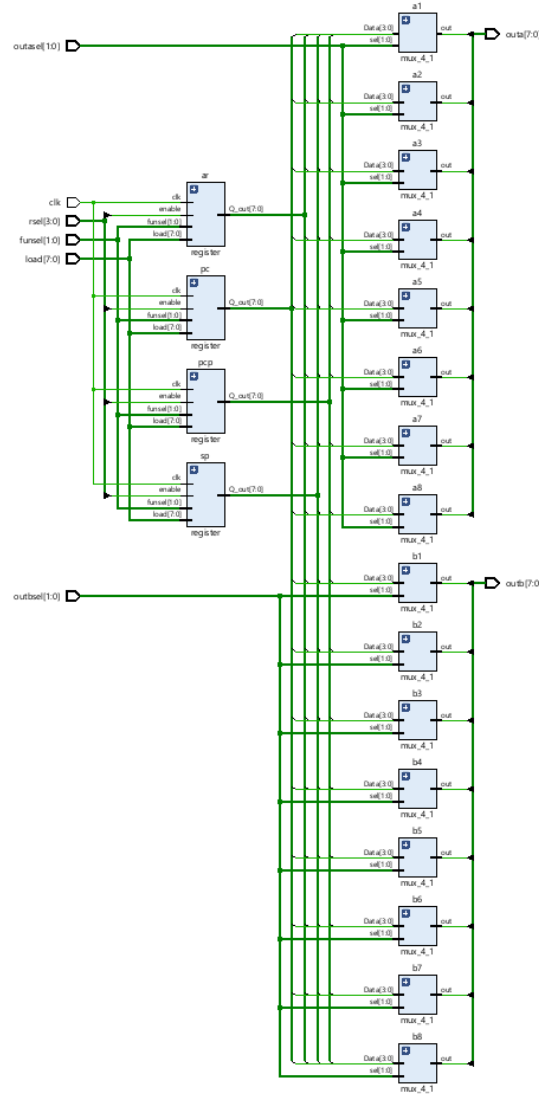


Figure 1: ARF System Design

3.2 Part 3

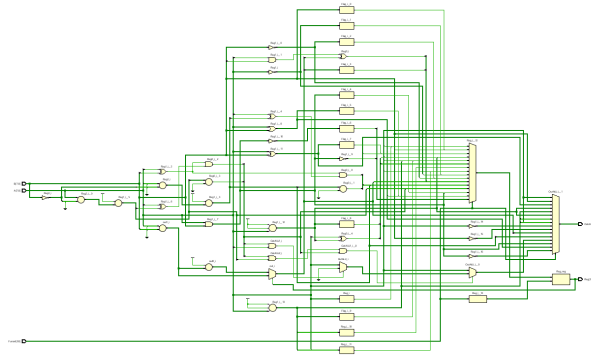


Figure 2: ALU Design

3.3 Part 4

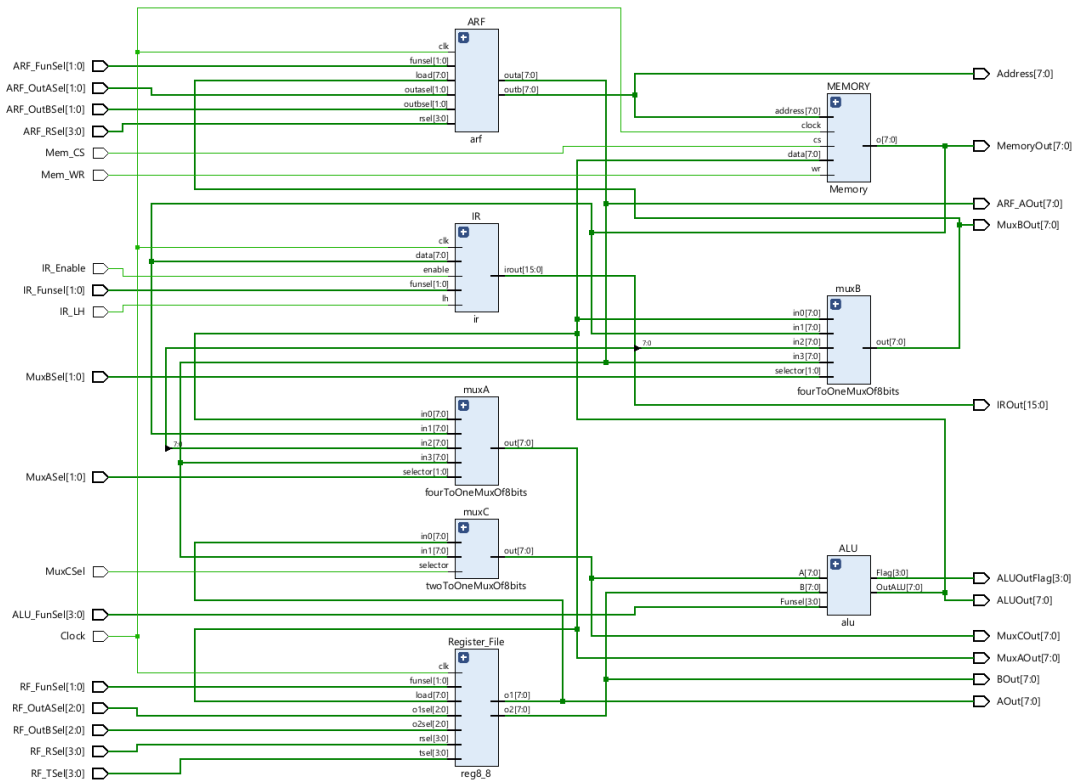


Figure 3: ALU System Design

4 RESULTS

4.1 Part 2

4.1.1 Part 2.c

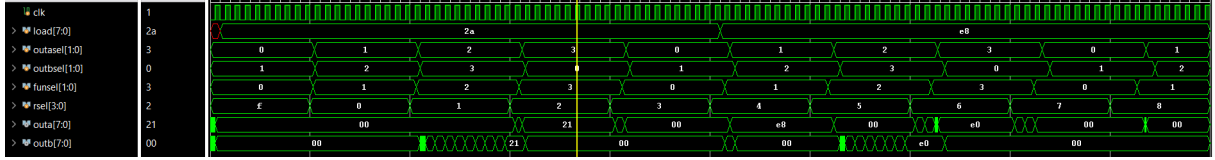


Figure 4: ARF Simulation

4.2 Part 3

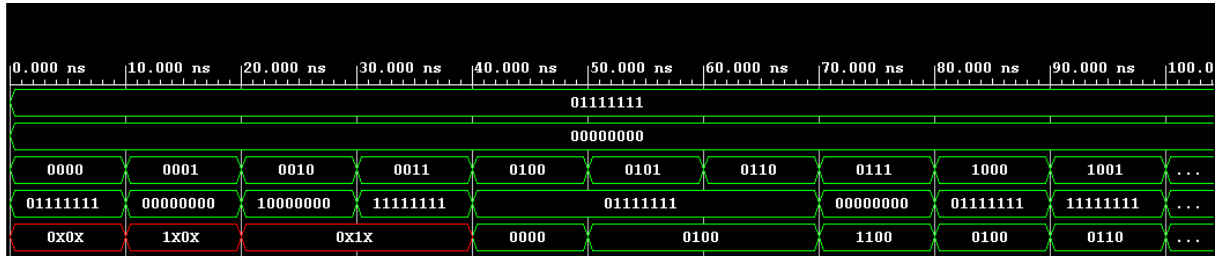


Figure 5: ALu Simulation, First Image

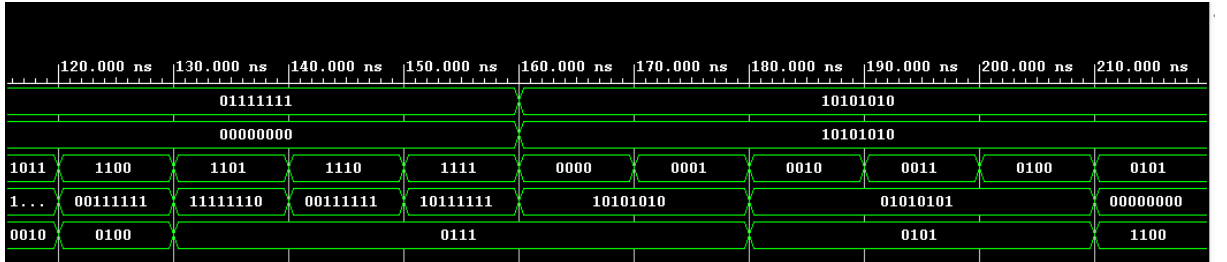


Figure 6: ALu Simulation, Second Image

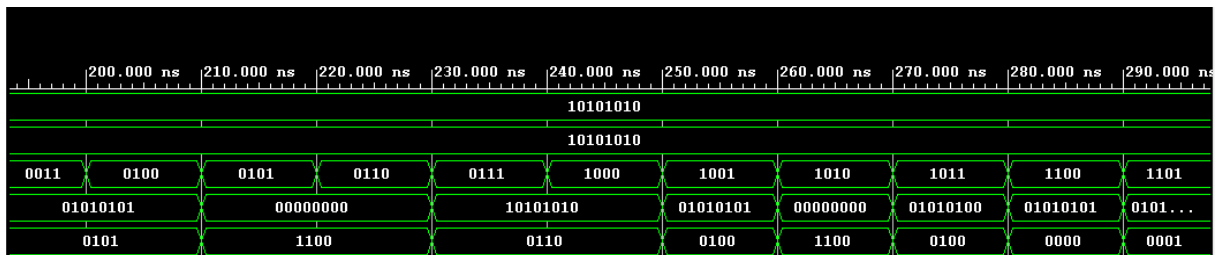


Figure 7: ALu Simulation, Third Image

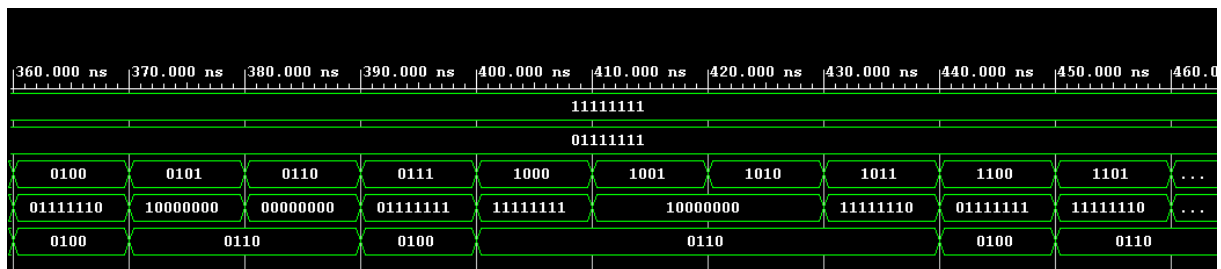


Figure 8: ALu Simulation, Fourth Image

4.3 Part 4

result of the part 4 is still controversial so we will wait for it.

5 CONCLUSION